

Interfacing 8085 µP with 7-Segment Display

Basic of 7 Segment Display :-


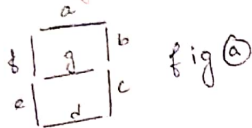


fig (a)

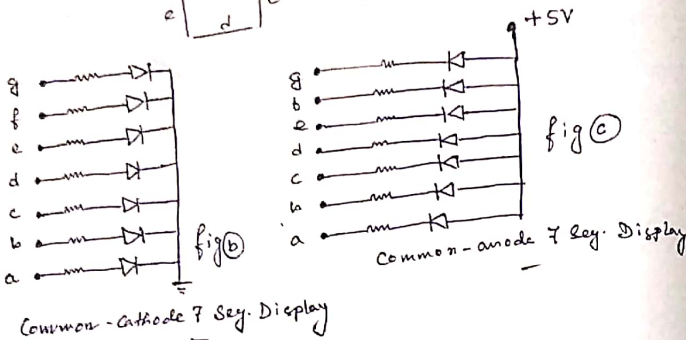

Common-Cathode 7 Seg. Display

7 Seg. display is multiple display using LED. It can display all decimal numbers and some letter. There are diff. some kind of LEDs in market like 9-segment LED, 14 segment LED...




- # There are two types of 7-segment display?
- Common Cathode — where +5V. d.c is applied to any segment to glow the corresponding LED. Similar to Active High i/p.
 - Common Anode — where 0V. or' Gnd connection is required to switch ON the corresponding LED. Similar to Active Low i/p.

These 7-segment display device is not connected directly with I/O Ports. They are connected using Decoder Or' Buffers.

FND 500, FND 503 — (Common Cathode) 7 Segment display.
FND 507, FND 570 — Common Anode.

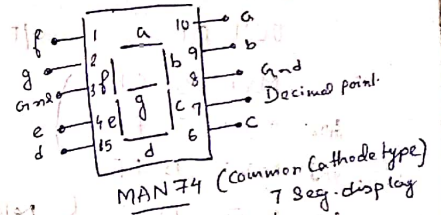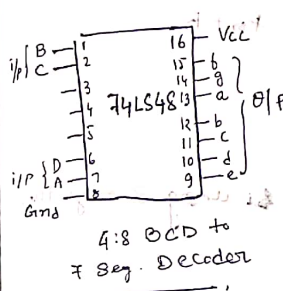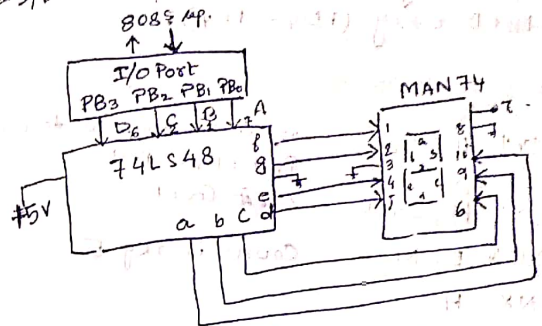(4:To 8 Decoder)

BCD to 7-seg decoder that is 74LS48 is used to interface bet. 7-seg display device & I/O port (8255). The fig of configuration is shown.



Here we can note following:

- Port B is used to send data to 74LS48 chip. (DCBA) this how data comes at BCD-7-seg display chip. Then, 8 o/p signals are generated according to the value of i/p. These 8 o/p signals of BCD-7-seg goes directly to MAN74 (Common Cathode type 7-seg. display) then corresponding LED will blink.

Then corresponding LED will blink.

Prog. MVI A 98H — [Control word as discussed in ADC Topic]
OUT 03 — Port B add: 01H. 05H data send to Port B. 0000 0101
MVI A 05H — Not used DCBA Bits
OUT 01 — In 4:8 Decoder, for i/p 0101, the o/p is 1
HLT

* If A, B, C, D value is ≥ 10 then Segment will display random figures.

* We can partially add another 7 segment display with Port B using (PB4 - PB7).

Write a program to display 0-9 decimal numbers.

Ans: MVI A, 98 Get Control word at Accumulator
 OUT 03 Initialize Port
 ABOVE: LXI H, 2500 Get Count
 JMOV E, M Count in reg E
 LOOP: INX H. Get next number
 MOV A M o/p at Port B.
 OUT 01
 MVI B 0F
 G02: MVI C FF
 G01: MVI D FF
 G0: DCR D
 JNZ G0
 DCR C
 JNZ G01
 DCR B
 JNZ G02
 DCR E Decrement Count
 JNZ LOOP Go to Loop to get next number
 JMP ABOVE Go ABOVE to restart.

Delay is using 3 registers.

Initial Data at following location

2500 - 0A (count value)	2505
2501 - 00	2506 - 05
2502 - 01	2507 - 06
2503 - 02	2508 - 07
2504 - 03	2509 - 08
2505 - 04	250A - 09

Interfacing 7-segment Display using Buffer:

Buffer 7407 is used here for interfacing. It has six o/p pins which can be used to give direct i/p to the Seven segment display chip. Here Port B is connected with buffer 7407 as given fig.



* As here we can directly give i/p to all segments of MAN74 chip so, the 7 segment representation Table is:

Digit	Hex Code Common Cathode	Hex Code Common Anode
0	3F	40
1	06	79
2	5B	24
3	4F	30
4	66	19
5	6D	12
6	7D	02
7	07	78
8	7F	80
9	67	18

Calculation: In case of BCD to 7seg. Decoder, we need not think about the i/p Hex code. we can give all valid BCD numbers (0...9) so that we will get corresponding display.

But here:

To display 3, the Hex code is 4F_H in Common Cathode 7-seg. That's how we calculate. in Common Anode Method

3₁₀ = 0011 in BCD

a	b	c	d	e	f
1	0	0	1	1	1
4	F _H				
011	000	000	0		
3					